

01. 0625\_s20\_MS\_61 Q: 2

2(a)(i)	$V_1 = 3.5$	1
2(a)(ii)	$I_1 = 0.38$	1
2(a)(iii)	$R_1 = 9.21$ (ecf allowed)	1
	Unit $\Omega$	1

(b)	$R_2 = 5.7$ and $R_3 = 4.6$ , with consistent 2 sf	1
(c)	Total $R = 20$	1
(d)	Statement matches readings (Expect B)	1
	Justification with suitable numbers quoted	1
(e)	Three lamps in series, correct symbol	1
	Voltmeter across lamp $L_3$	1
	Other symbols and circuit correct	1

02. 0625\_s20\_MS\_63 Q: 2

(a)(i)	correct voltmeter symbol in parallel with resistor	1
	correct ammeter symbol in series	1

(a)(ii)	$V_A = 2.4$ (V)	1
	$I_A = 0.48$ (A)	1
(a)(iii)	correct calculation of $R_A = 5(.0)$ / ecf	1
(b)	correct unit for $R - \Omega$	1
(c)	all $R$ values to consistent 2 or consistent 3 significant figures	1
(d)	statement matching results	1
	justification matching statement with <u>values</u> from results used, e.g. within limits of experimental accuracy	1
(e)(i)	correct symbol for potentiometer	1
(e)(ii)	can obtain average value / plot a graph	1

03. 0625\_s19\_MS\_63 Q: 3

(a)	correct voltmeter symbol in parallel with X	1
(b)	$I = 0.22$ (A)	1
	$V = 1.1$ (V)	1
	A, V, $\Omega$	1
(c)	statement matching results <u>and</u> 'currents the same within limits of experimental accuracy' / owtte	1
(d)(i)	R values 5.0/ecf, 14(.3478), 24/(23.8095) ( $\Omega$ )	1
	consistent 2 or consistent 3 sig figs	1
(d)(ii)	$R_V = 9.0$ ( $\Omega$ ) <u>and</u> $R_Z = 10$ ( $\Omega$ )	1
(e)(i)	3 resistors in parallel arrangement <u>and</u> circuit symbols correct	1
	voltmeter and ammeter in correct arrangement <u>and</u> circuit symbols correct	1
(e)(ii)	$10R_P = R_S$	1

04. 0625\_w19\_MS\_61 Q: 2

(a)(i)	$V = 2.5$	1
	$I = 0.3(0)$	1
	Both units correct	1
(a)(ii)	$R_1$ 8.33 (ecf allowed)	1
(b)	$R_2$ 11.4 with unit $\Omega$	1
(c)	Statement matches results	1
	Justification matches statement	1
(d)	Lamps in parallel and correct symbol for lamp	1
	One voltmeter, with correct symbol, in parallel with lamps	1
	Variable resistor in correct position, with correct symbol	1

05. 0625\_m18\_MS\_62 Q: 3

(a)	correct voltmeter symbol in parallel with lamp X	1
(b)	$I_s = 0.34$ (A)	1
(c)(i)	$V_x = 1.2$ (V) <u>and</u> $V_y = 1.9$ (V)	1
(c)(ii)	$V_s$ present <u>and</u> correct units (A, V) seen in (b) and (c)	1
(c)(iii)	statement matching results	1
	justification matching statement with <u>use of comparative values</u> (e.g. 3.1 and 3.0 are within limits of experimental accuracy)	1
(d)	correct calculation of $R_1$ (3.5 / ecf)	1
(e)(i)	lamps in parallel arrangement	1
	all circuit elements in correct arrangement and all circuit symbols correct	1
	resistance increases with temperature	1
(e)(ii)	$R_2 > R_1$ <u>and</u> brighter lamp has higher temperature	1

06. 0625\_s18\_MS\_61 Q: 2

(a)(i)	EITHER $V_1 = 2.2$ OR $I = 0.46$ correct	1
	Both values correct <u>and</u> correct units V and A	1
(a)(ii)	$R_1 = 4.78$ ( $\Omega$ ) (allow ecf from 2(a)(i))	1
(b)	Statement matches readings (Expect YES)	1
	Expect justification to include the idea of within the limits of experimental accuracy (but accept beyond limits, if ecf allowed for statement matching readings)	1
(c)	$R = 14.3$ OR 14.4; 2 or 3 significant figures required	1
	Unit $\Omega$	1
(d)	$3V_1$	1
(e)	3 resistors in parallel	1
	Correct variable resistor symbol	1
	Voltmeter symbol correct <u>and</u> circuit correct	1

Paper Perfection, Crafted With Passion

07. 0625\_w18\_MS\_62 Q: 2

(a)(i)	$V_T = 2.5(0)$ (V)	1
	$I_T = 0.18(0)$ (A)	1
(a)(ii)	0.45 (W)	1
(b)(i)	$P_X = 0.23$ , $P_Y = 0.22$ and unit W	1
(b)(ii)	statement: Yes idea of within the limits of experimental accuracy	1
	<b>explained:</b> e.g. close enough, very close, not too far apart	1
(c)	statement: disagree / no	1
	low current not sufficient to make lamp glow / first lamp would not glow with no current / since there is a current (other lamp cannot be broken).	1
(d)	lamps and voltmeter in parallel	1
	correct symbols for lamps, ammeter and voltmeter	1
	variable resistor, correct symbol and position in a correct circuit	1

08. 0625\_w17\_MS\_61 Q: 1

(a)(i)	1.8 (V)	1
	0.38 (A)	1
(a)(ii)	$R_1$ 4.74 (4.737, 4.7)	1
(b)	$R_2 = 9.47$ OR 9.5 (2 or 3 significant figures required)	1
(c)	Pointer at 0.13	1
(d)	Statement YES or NO (owtte) Justification to include the idea of within (or beyond, ecf) the limits of experimental accuracy, matching the statement	1
(e)	Determine each resistance in turn	1
(f)	Three resistors in parallel, ONE voltmeter in parallel with resistors and correct symbols for voltmeter and resistors	1
	Variable resistor in series with the supply, correct symbol in a correct circuit	1
(g)	Repeat with different currents OR to obtain a range of readings	1

09. 0625\_w17\_MS\_63 Q: 2

(a)	correct voltmeter symbol in parallel with X	1
(b)	$I_S = 0.18$ (A)	1
(c)(i)	$V_X = 1.2$ (V) AND $V_Y = 2.3$ (V)	1
(c)(ii)	correct units (A, V) seen in (b) and (c)	1
(c)(iii)	statement matching readings	1
	justification, with use of values seen, matching readings and statement e.g. '3.5 V and 3.7 V are within limits of expt accuracy'	1
(d)	correct calculation of $R_s$ (20.6)	1
	2 / 3 sig figs and unit( $\Omega$ )	1
(e)(i)	resistors in parallel with correct symbol	1
	rest of circuit correct	1
(e)(ii)	valid suggestion AND explanation consistent with results	1

10. 0625\_s16\_MS\_63 Q: 4

(a)	correct voltmeter symbol in parallel with lamp <b>P</b>	1
(b)	$I = 0.23$	1
	unit of A	1
(c)	$V_P = 2.7$ and $V_Q = 0.3$	1
(d)(i)	some current in the circuit, pd across lamp <b>Q</b> is small / not equal to supply voltage / reference to lamp <b>P</b> bright <u>and is in series</u>	1
(d)(ii)	$V_P$ greater than / near working voltage	1
	$V_Q$ <u>much</u> less than working voltage	1
(e)	$R = 13(.0)$ allow ecf	1
	2/3sig figs and unit of $\Omega$	1
(f)	statement matches results	1
	some correct values used and reference to 'within limits of experimental accuracy' / owtte	1
		<b>Total: 11</b>

11. 0625\_w16\_MS\_61 Q: 4

	<b>MP1</b> On circuit diagram: one voltmeter in parallel with any component	1
	<b>MP2</b> Circuit diagram correctly shows power supply, ammeter, unless in a branch, two or more resistors in parallel	1
	<b>MP3</b> Circuit diagram: Correct symbols for ammeter, voltmeter and fixed resistor	1
	<b>MP4</b> Repeat with a different number of resistors (in parallel)	1
	<b>MP5</b> Table that includes columns for number of resistors, voltage/V and current/A	1
	<b>MP6 &amp; MP7</b> Then any two from: Resistance calculated (may be shown in table) Use low current (to stop resistors getting too hot)/switch off between readings  Use at least 5 different combinations Repeat with different current or voltage or variable resistor setting Drawing a graph of number of resistors against combined resistance	2
		<b>Total: 7</b>

12. 0625\_s15\_MS\_61 Q: 3

- (a) (i)  $V = 1.8$  [1]  
 $I = 0.25$  AND both units correct, V and A [1]  
 (ii)  $R_S$  calculated correctly, e.c.f. (i), expect  $7.2 (\Omega)$  [1]
- (b) (i) lamps in parallel and ammeter in a correct position [1]  
 voltmeter in correct position, with rest of circuit and symbols correct [1]  
 (ii)(iii)  $R_P = 3.3$  or  $3.33$  with unit  $\Omega$  and 2 or 3 significant figures AND  $R_S/R_P$  calculated [1]
- (c) (i) voltage or p.d., accept current [1]  
 (ii) adjust power supply OR add resistor/variable resistor [1]

**[Total: 8]**

13. 0625\_s15\_MS\_62 Q: 3

- (a) (i)  $V = 2.4(0)(V)$  [1]  
 $I = 0.84 (A)$ , both units correct [1]  
 (ii)  $R_P = 2.86$  OR  $2.9 (\Omega)$  ecf (a)(i) [1]
- (b) lamps in series [1]  
 voltmeter and ammeter in correct position, with rest of circuit and symbols correct [1]
- (c)  $R_S = 11.4$  OR  $11 (\Omega)$  NOT more than 3 sig. figs. [1]
- (d) (i) correct symbol for variable resistor NOT potentiometer [1]  
 (ii) X correctly positioned [1]

**[Total: 8]**

14. 0625\_w15\_MS\_62 Q: 3

- (a) (i)  $V_1 = 2(.0)$  (V) [1]  
 $I_1 = 0.32$  (A) [1]
- (ii)  $R_1 = 6.25$  ( $\Omega$ ) OR e.c.f. (i) AND correct units V, A,  $\Omega$  in (i) and (ii) [1]
- (b) correct arrangement of resistors [1]  
correct position for voltmeter AND correct circuit symbols AND correct labelling of resistors **A**, **B** and **C** [1]
- (c) (i) 3.0/3.04/3.043 ( $\Omega$ ) [1]
- (ii) 2.1/2.05/2.06/2.07/2.08 OR e.c.f. AND no unit [1]
- (d) statement matches results [1]  
justification including the idea of within (or beyond) the limits of experimental accuracy [1]

[Total: 9]

---

15. 0625\_w15\_MS\_63 Q: 4

- (a) correct symbol for voltmeter AND shown connected in parallel [1]
- (b) 3(.0)(V) AND 0.38(A) [1]
- (c) arrows showing 2.8–3.0 V AND 0.76–0.78 A [1]
- (d)  $R_1 = 7.9$  (OR e.c.f.),  $R_2 = 3.8$ ,  $R_3 = 2.7$  [1]  
correct unit (symbol or word) [1]  
consistently 2 sig. figs. OR consistently 3 sig. figs. [1]
- (e) (i) statement matches results with any relevant values quoted [1]  
justification matching statement [1]
- (ii)  $R_3$  should be  $\frac{1}{3} \times R_1$  owtte [1]

[Total: 9]

16. 0625\_w14\_MS\_63 Q: 5

- (a) voltmeter in parallel with lamp **L** and with correct symbol [1]
- (b)(c) table:  
 $V = 1.7$  (V) [1]  
 $I = 0.18$  (A) [1]  
 $R = 9.4(4)$  ecf (b), 7.6/7.58 with 2 or 3 sig. figs. [1]  
 all units correct (V, A,  $\Omega$ ) [1]
- (d) statement matches results, with matching justification which refers to values being 'too different' / 'difference beyond limits of experimental accuracy' owtte [1]
- (e) lamp in circuit 1 brighter than in circuit 2  
and has greater resistance [1]
- (f) correct circuit symbol for variable resistor (rectangle with strike-through arrow only) [1]  
 connected in correct series circuit [1]

[Total: 9]

17. 0625\_s13\_MS\_62 Q: 3

- (a) (i)  $V_1 = 0.7$  (V) [1]  
 $I = 0.45$  (A) [1]
- (ii)  $R_1 = 1.56$  or  $1.6$  ( $\Omega$ ) e.c.f. (i) [1]
- (b)  $V_2 = 0.6$  (V) and  $V_3 = 0.5$  (V) c.a.o. [1]
- (c)  $1.8$  (V) e.c.f.  $V_1, V_2, V_3$  [1]
- (d) correct symbols for ammeter, lamp, voltmeter [1]  
 correct parallel circuit with ammeter and voltmeter correctly connected [1]
- (e) statement matches candidate's results and idea of within/beyond limits of experimental accuracy or that values are too far apart / too different [1]
- (f) brighter [1]

[Total: 9]

18. 0625\_s13\_MS\_63 Q: 3

- (a) correct symbol for voltmeter [1]
- (b) (i) 2.59, 8.00, 3.91 [1]  
consistent 2 or 3 sig. figs. [1]
- (ii) units all correct (symbols or words) [1]
- (c) statement matches result (expect 'No') [1]  
*R figures* quoted appropriately and matching statement  
(need to see too different o.w.t.t.e.) [1]
- (d) correct parallel connection [1]

[Total: 7]

19. 0625\_w13\_MS\_61 Q: 3

- (a) (i) 1.8 (V) [1]  
0.3 (A) [1]
- (ii)  $P_1 = 0.54$  (W) e.c.f. allowed [1]
- (iii)(iv)(v)  $P_T = 1.59$  (or 1.6) W [1]
- (b) statement matches results (expect YES) e.c.f. allowed [1]  
justification in terms of within or beyond limits of experimental accuracy o.w.t.t.e. [1]
- (c) (i) diagram: [1]  
lamps in parallel, variable resistor in series with power supply, with correct symbols  
for variable resistor, lamps and voltmeter [1]  
one voltmeter correctly positioned [1]
- (ii) vary current (or p.d.) [1]

[Total: 9]

20. 0625\_s12\_MS\_63 Q: 3

- (a) (i)  $V_1 = 1.9$  [1]  
 $I_1 = 0.3$  [1]  
 Units V and A both correct [1]
- (ii)/(iii)  $R_P = 6.33$  and  $4R_P = 25.3/25.2$  to 2 or 3 sig. figs. [1]  
 $\Omega$  [1]
- (b)  $R_S = 23.8 (\Omega)$  or  $24 (\Omega)$  [1]
- (c) Correct statement (from candidate's work) [1]  
 with matching justification (idea of within or beyond experimental accuracy)
- (d) Circuit: correct symbols for ammeter, voltmeter and lamp in correct series circuit [1]
- (e) (i) Change/control current/voltage [1]  
 (ii) To obtain range of readings (or wtte) [1]
- [Total: 10]**

91. 0625\_w12\_MS\_61 Q: 3

- (a) Correct symbols for ammeter, voltmeter and lamps [1]  
 Ammeter and voltmeter in correct positions [1]  
 Correct parallel circuit [1]
- (b) (i) and (ii)  $V_A = 1.9(V)$   $R_A = 2.9(2) (\Omega)$  [1]  
 Units V and  $\Omega$  [1]
- (iii) Pointer at correct position (0.65) [1]
- (c) No mark awarded
- (d) Statement matches readings (expect YES) [1]  
 Justified with idea of experimental inaccuracy [1]  
 (expect 'close enough', owtte)
- [Total: 8]**

22. 0625\_w12\_MS\_62 Q: 3

- (a) Voltmeter symbol and position correct [1]
- (b) Pointer in correct position [1]
- (c) (i)  $I_1 = 0.84\text{ A}$ ,  $I_2 = 0.33\text{ A}$ ,  $I_3 = 0.50\text{ A}$ , all correct no significant figures penalty  
Unit at least once and not contradicted [1]
- (ii) No mark awarded
- (iii) Sensible comment about experimental inaccuracy  
e.g. difficulty in reading meter/scale or meter has a zero error [1]
- (d) Circuit: correct symbol for variable resistor (not potential divider) [1]  
Variable resistor in a correct position [1]
- (e) Workable solution, e.g. short circuit each in turn/exchange of lamp from other circuit  
branch/put lamps in parallel and check/use voltmeter to check pd across bulbs plus what  
is observed [1]

[Total: 7]

---



**Ace | GCSE**  
Paper Perfection, Crafted With Passion