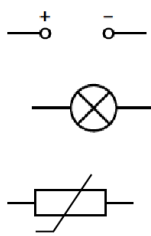


01. 0625\_m23\_ms\_42 Q: 7

Question	Answer	Marks
(a)	work done in passing charge <u>through / across</u> a component	B1
	work done per unit charge	B1
(b)(i)	(definition of emf:) $E = W/Q$	B1
(b)(ii)	270 J	A2
	$W = EQ$ OR $9.0 \times 30$	(C1)

Question	Answer	Marks
(c)(i)	correct symbols for d.c. power supply, a lamp and a thermistor  	B1
	three components in a complete series circuit	B1
(c)(ii)	resistance (of thermistor) decreases (when temperature increases)	B1
	resistance of <u>circuit</u> decreases OR greater current (in lamp so brightness of lamp increases) OR greater p.d. across <u>lamp</u> (so brightness of lamp increases)	B1

02. 0625\_s23\_ms\_41 Q: 7

Question	Answer	Marks
(a)	any <b>two</b> from: <ul style="list-style-type: none"> <li>(potential divider) splits / shares / divides the e.m.f. / voltage / potential difference / p.d. (of a power source / in a circuit)</li> <li>(e.m.f. is) split between (two) resistors / components (connected in series to power source)</li> <li>(potential divider shares e.m.f.) in proportion to the resistances (of the resistors / components)</li> </ul>	B2
(b)(i)	(e.m.f. =) 15 V	B1
(b)(ii)	(resistance =) 60 $\Omega$	A3
	$(R_{11} =) R_2 R_3 / (R_2 + R_3)$ OR $(R_{11} =) 40 \times 40 / (40 + 40)$ OR $(R_{11} =) 1600 / 80$ OR $1/R_{11} = 1/R_2 + 1/R_3$ OR $1/R_{11} = 1/40 + 1/40$ OR $(R_{11} =) (1/40 + 1/40)^{-1}$ OR $(R_{11} =) 20 (\Omega)$	C1
	(resistance =) 40 + (candidate's value for combined resistance of $R_2$ and $R_3$ )	C1

Question	Answer	Marks
(c)	(reading =) 10 V	A2
	emf shared in same proportion as resistance OR e.g. $R_1 / R_{11} = V_1 / V_{11}$ OR (reading =) $15 \times 40 / 60$ OR (reading =) $0.25 \times 40$	C1

03. 0625\_s23\_ms\_42 Q: 8

Question	Answer	Marks
(a)(i)	region in which a (magnetic) pole experiences a force	B1
(a)(ii)	in the direction of the force on the N pole	B1

Question	Answer	Marks
(b)	4 radial lines outside sphere, touching the sphere and equally spaced all around sphere	B1
	direction of arrows towards the sphere	B1
(c)(i)	2.0V	A1
(c)(ii)	(ratio of p.d. across $R_2 : R_3 =$ ) 1 : 2	B1
(c)(iii)1.	current is zero in $R_1$ AND diode is in wrong direction (to allow current) owtte	B1
(c)(iii)2.	(ratio of p.d. across $R_2 : R_3 =$ ) 1 : 1	B1

04. 0625\_w23\_ms\_41 Q: 8

Question	Answer	Marks
(a)(i)	900 C	A2
	$I = Q/t$ OR ( $Q =$ ) $It$ OR $1.5 \times 600$	C1
(a)(ii)	2.0 $\Omega$	A3
	$R = V/I$ OR ( $R_{\text{tot}} =$ ) $V/I$ OR $9.(0)/1.5$ or $6.(0)$	C1
	( $R_{\text{cyl}} =$ ) total resistance – P OR ( $R_{\text{cyl}} =$ ) $6.0 - 4.0$	C1
(b)	1200 s	A4
	$R$ is directly proportional to $l$ OR (new cylinder) twice as long means twice $R$	C1
	$R$ is inversely proportional to $A$ OR (new cylinder) half cross-sectional area means twice $R$	C1
	(resistance of cylinder $=$ ) $4 \times$ (a)(ii) ( $\Omega$ )	C1

05. 0625\_w23\_ms\_42 Q: 6

Question	Answer	Marks
(a)	(p.d. across LED = $4.5 - 1.2 =$ ) 3.3 V	A2
	( $V =$ ) $IR$	C1
(b)	LED (is a diode, which) only allows current in one direction / has a very high resistance (when direction of current is reversed.) OR (it) is reverse-biased	B1
(c)	$E=IVt$ OR ( $t =$ ) $E / VI$ OR $Q = E / V$ AND $Q = I \times t$	B1
	( $t =$ ) $1050 \div [0.02 \times 4.5 \times 3600]$ OR ( $t =$ ) 3.2 h	B1
(d)	(charge $=$ ) 72 C	A2
	$I = Q/t$ OR ( $Q =$ ) $It$ OR ( $Q =$ ) $0.02(0) \times 3600$	C1

06. 0625\_w23\_ms\_43 Q: 6

Question	Answer	Marks
(a)	<u>sketch:</u> one axis labelled $V$ and the other labelled $I$ , either way round AND gradual curve from origin curving such that $V/I$ increases	<b>B1</b>
	<u>explanation:</u> (as current / temperature increases so) resistance increases	<b>B1</b>
	(so) more voltage required for same increase in current owtte <b>OR</b> if $V$ on $y$ -axis: gradient must increase <b>OR</b> if $V$ on $x$ -axis: gradient must decrease	<b>B1</b>
(b)(i)	9.0 V	<b>A2</b>
	12.0 – 3.0	<b>C1</b>
(b)(ii)	2.1 A	<b>A2</b>
	$I = V/R$ <b>OR</b> ( $I =$ ) $V/R$ <b>OR</b> 9.0/4.2	<b>C1</b>
(b)(iii)	0 (A)	<b>A1</b>
(b)(iv)	(ammeter reading) 2.1 A	<b>A1</b>
(b)(v)	19 W	<b>A2</b>
	$P = VI$ <b>OR OR</b> ( $P =$ ) $VI$ <b>OR</b> $9 \times 2.1$	<b>C1</b>

07. 0625\_m22\_ms\_42 Q: 7

Question	Answer	Marks
(a)	8 (cells)	<b>B1</b>
(b)(i)	$(12/2.4 =) 5.0 \Omega$	<b>A2</b>
	$R = V/I$ in any form	<b>(C1)</b>
(b)(ii)	(Resistance of Q = $5 - 1.5$ ) = $3.5 \Omega$	<b>A2</b>
	$1/R = 1/R_1 + 1/R_2$ <b>OR</b> $R = R_1R_2/(R_1+R_2)$	<b>(C1)</b>

Question	Answer	Marks
(c)(i)	correct voltmeter symbol connected correctly across both lamps	<b>B1</b>
(c)(ii)	4.3 W	<b>A3</b>
	( $P =$ ) $IV$ in any form <b>OR</b> $1.2 \times 3.6$	<b>(C1)</b>
	3.6 V <b>OR</b> 1.2 A	<b>(C1)</b>

08. 0625\_s22\_ms\_42 Q: 9

Question	Answer	Marks
(a)(i)	0 (A)	B1
(a)(ii)	$(I = 12/2 =) 6.0 \text{ A}$	A2
	$(I =) V/R$ in any form	C1
(a)(iii)	$(I = 12/5 =) 2.4 \text{ A}$	A2
	$(R_s = R_1 + R_2 = 2 + 3 =) 5 (\Omega)$	C1
(b)	$(R_p = 6/5 =) 1.2 \Omega$	A3
	$1/R_p = 1/R_1 + 1/R_2$ OR $(R_p =) R_1 R_2 / (R_1 + R_2)$	C1
	$1/R_p = 1/2 + 1/3$ OR $(R_p =) 2 \times 3 / (2 + 3)$	C1

09. 0625\_s22\_ms\_43 Q: 8

Question	Answer	Marks
(a)(i)	light-dependent resistor / LDR	B1
(a)(ii)	voltmeter connected in parallel with component Y	B1
(a)(iii)	1 0.016 A	A2
	$(I =) V/R$ in any form or $12/400$ or $12/350$ or $12/750$ OR $(R_{\text{total}} = R_1 + R_2 =) 750 (\Omega)$	C1
	2 6.4 V	A1
(a)(iv)	(in a dark room the p.d. across component Y) decreases	B1
(b)	one named practical application of LDR e.g. switch on street lights (at night) / turn on security light (at night)	B1


10. 0625\_w22\_ms\_41 Q: 8

Question	Answer	Marks
(a)	both relate to energy per unit charge	B1
(b)	e.m.f. applies to the whole circuit / source or p.d. to one (or more) component or energy conversion to electrical for e.m.f. or from electrical for p.d.	B1
(c)(i)	4.8 V	B1
(c)(ii)	20 $\Omega$	A3
	$1/R_T = 1/R_1 + 1/R_2$ or $(R_T =) R_1 R_2 / (R_1 + R_2)$ or $1/R_T = 1/24 + 1/12$ or $1/R_T = 3/24$ or $(R_T =) 24 \times 12 / (24 + 12)$	C1
	8.0 ( $\Omega$ )	C1
(c)(iii)	2.9 V	A2
	$V = ER/R_T$ in any form or $4.8 \times 12/20$ or $I = E/R$ in any form or 0.24 seen	C1

11. 0625\_m21\_ms\_42 Q: 8

	Answer	Marks
(a)	energy supplied by a source in driving charge around a complete circuit / energy needed to drive unit charge / 1 coulomb round circuit	B1
(b)(i)	$(P=) 90 \text{ W}$	A3
	$(P=) VI$ in any form	C1
	$(V/R \text{ OR } I =) 2$	C1
(b)(ii)	(p.d. =) 15 V	A2
	(p.d. =) 60–45	C1
(b)(iii)	$(I = 15 / 10 =) 1.5 \text{ A}$	A2
	$(I =) V/R \text{ OR } V = IR$ in any form	C1

12. 0625\_s21\_ms\_41 Q: 8

	Answer	Mark
(a)	 and between P and Q	B1
(b)	1.5 V c.a.o.	B1
(c)(i)	1600 $\Omega$	A3
	$(V_{800 \Omega} =) 4.0 \text{ (V)}$	C1
	$(I =) V/R$ in any form or 4.0 / 800 or 0.0050 (A) or $(R =) V/I$ or 8.0 / 0.0050	C1
	OR 1600 $\Omega$	(A3)
	$(V_{800 \Omega} =) 4.0 \text{ (V)}$	(C1)
	$(R_{Th} =) R_{800 \Omega} \times V_{Th} / V_{800 \Omega}$ in any form or $(R_{Th} =) 800 \times 8.0 / 4.0$ in any form	(C1)
	OR 1600 $\Omega$	(A3)
	$\frac{12}{800+R_{Th}}$ or $\frac{8.0}{R_{Th}}$ or $\frac{R_{Th}}{800+R_{Th}}$	(C1)
$\frac{12}{800+R_{Th}} = \frac{8.0}{R_{Th}}$ in any form	(C1)	

	Answer	Mark
(c)(ii)	larger proportion of the e.m.f. (across thermistor) or smaller voltage across 800 $\Omega$	B1
	temperature (of thermistor) is smaller / has decreased	B1
	resistance of thermistor / circuit is large(r)	B1

13. 0625\_s21\_ms\_42 Q: 10

	Answer	Mark
(a)	$V = IR$ in any form or $(R =) V/I$	C1
	$(R = 9.2 / 0.004 =) 2300 \Omega$	A1

	Answer	Mark
(b)	(much) greater current in lamp OR lamp activated / lights / glows / gets brighter owtte	B1
	resistance of thermistor / component / K reduced (compared to value at (very) low temperature)	B1
	voltage / p.d. of point X / across R increases	M1
	(larger) current in lamp	A1
(c)	thermistor	B1

14. 0625\_s21\_ms\_43 Q: 7

	Answer	Mark
(a)	energy supplied	M1
	to drive a unit charge / 1 C round a complete circuit	A1
(b)(i)	$(R =) 2.3 \Omega$ OR $2.2 \Omega$	A3
	$R = V/I$ in any form	C1
	current in R = 4 (A) OR p.d. across R = 9 (V)	C1
(b)(ii)	$1.1 \Omega$	A3
	resistance proportional to length (so twice length twice resistance)	C1
	resistance inversely proportional to area (so twice diameter decreases resistance by factor of 4)	C1

15. 0625\_w21\_ms\_41 Q: 8

Question	Answer	Marks
(a)	$Q/t$ or (rate of) flow of (electric) charge / electrons	B1
(b)	(current in the $450 \Omega$ resistor =) ..... $I_2 - I_1$ .....	B1
(c)	$(V_{450 \Omega} =) IR$ or $0.012 \times 450$ or $5.4 (V)$ or $9.0 - 5.4$ or $3.6 (V)$ seen	C1
	$(I =) 3.6 / 800$ or $0.0045 (A)$	C1
	$(P =) VI$ or $3.6 \times 0.0045$ or $3.6^2 / 800$	C1
	$1.6 \times 10^{-2} W$ or $16 mW$	A1
(d)	resistance (of LDR) decreases	B1
	current (in circuit) increases      or      resistance of parallel pair decreases	C1
	p.d. across $800 \Omega$ resistor increases and p.d. across $450 \Omega$ resistor decreases      or      resistance of parallel pair a smaller fraction of total resistance and p.d. across $450 \Omega$ resistor decreases	A1

16. 0625\_w21\_ms\_42 Q: 9

Question	Answer	Marks
(a)	7.5 V	B1
(b)(i)	$1/R_p = 1/R_1 + 1/R_2$ OR $(R_p =) R_1R_2/(R_1 + R_2)$ in any form	C1
	$(R_p =) 1.2 (\Omega)$	C1
	3.2 $\Omega$	A1
(b)(ii)	$(V =) IR$ in any form	C1
	4.1 V	A1

17. 0625\_w21\_ms\_43 Q: 9

Question	Answer	Marks
(a)(i)		B2
	four components joined in series	B1
	all circuit symbols correct for resistor, thermistor, a filament lamp and a power supply	B1
(a)(ii)	voltmeter connected in parallel to the resistor	B1
(a)(iii)	(p.d. across terminals of power supply) = 18 V	A4
	(current through resistor when p.d. across it is 6.0 V =) 0.4 A	C1
	current same through all components in series circuit OR horizontal line through 0.4 A on graph through all three curves OR p.d. across filament lamp = 3.0 V OR p.d. across thermistor = 9.0 V	C1
	p.d. across filament lamp = 3.0 V AND p.d. across thermistor = 9.0 V	C1
(b)	any sensible use requiring temperature control or depending on temperature, e.g. fire alarms, to keep computers cool (by operating fan), in incubators, electronic thermometer, electronic thermostat in kettle / car engine	B1

18. 0625\_m20\_ms\_42 Q: 8

(a)	$\{R_s = R_1 + R_2 + R_3$ in any form OR $(R_s) = R_1 + R_2 + R_3$ OR $(R_s) = 3 + 2 + 6 (\Omega)$ OR $(R_s) = 11 (\Omega)\}$ AND $\{V = IR$ in any form OR $(I =) V / R$ OR $(I =) 12 / 11 (A)\}$	C1
	$(I =) 1.1 A$	A1
(b)	uses resistance of wire proportional to length OR (resistance $XQ =$ ) 6 $\Omega$ 0.6 / 2.0 ( $\Omega$ ) OR 1.8 ( $\Omega$ )	B1
	$1/R_p = 1/R_1 + 1/R_2$ OR $(R_p =) R_1R_2 / (R_1 + R_2)$	C1
	$1/R_p = 1/1.5 + 1/(6 \times 0.6/2)$ OR $(R_p =) 1.5 \times (6 \times 0.6/2) / (1.5 + 6 \times 0.6/2)$ OR $(R_p =) 1.5 \times 1.8 / \{1.5 + 1.8\} = 0.82 (\Omega)$	C1
	$(R = 3 + 2 + 0.82 =) 5.8 \Omega$	A1

19. 0625\_s20\_ms\_41 Q: 8

(a)	990 / (54 / 1.2) OR 990 / 45 OR (number of cells in pack =) 54 / 1.2 OR 45	<b>C1</b>
	22	<b>A1</b>
(b)(i)	$(P =) EI$ OR $1.2 \times 3.5$	<b>C1</b>
	4.2 W OR 4.2 J / s	<b>A1</b>
(b)(ii)	thick wires have a smaller resistance	<b>B1</b>
	less thermal energy generated in wires	<b>B1</b>
	more efficient OR less risk of fire / insulation melting	<b>B1</b>

20. 0625\_s20\_ms\_42 Q: 8

(a)	two circuit symbols correct	<b>B1</b>
	three circuit symbols correct	<b>B1</b>
	symbol for cell, battery or power supply AND two other circuit symbols in series	<b>B1</b>
	LED correct way round	<b>B1</b>
(b)	$R = V / I$ in any form OR $(R =) V / I$	<b>C1</b>
	$(R = 3.1 / 0.030 =) 100 \Omega$	<b>A1</b>
(c)(i)	uses $10.5 = 2.1 + V$ across heater	<b>C1</b>
	$(R = 8.4 / 1.5 =) 5.6 \Omega$	<b>A1</b>
(c)(ii)	$P = VI$ in any form OR $(P =) VI$	<b>C1</b>
	$(P = 8.4 \times 1.5 =) 12.6 \text{ W}$	<b>A1</b>

21. 0625\_w20\_ms\_42 Q: 10

Question	Answer	Marks
(a)(i)	recognisable ammeter in gap AB AND straight lines in CD AND EF	B1
(a)(ii)	recognisable voltmeter across $4\ \Omega$	B1
	correct voltmeter symbol used	B1
(a)(iii)	$V = IR$ in any form or $(V =) IR$ words, symbols or numbers	C1
	$(V_{2\Omega} = 2 \times 2.5 =) 5\text{ V}$	C1
	$(I_{4\Omega} = 5 \div 4 =) 1.3\text{ A}$ must be clear that $I$ refers to $4\ \Omega$ OR calculates $R_p = 1.33\ \Omega$ OR $4 \div 3\ \Omega$	C1
	$(I_{6\Omega} = 2.5 + 1.3 =) 3.8\text{ A}$ OR $(I_{6\Omega} = 5 \div 1.33 =) 3.8\text{ A}$	A1
	Alternative route for first 3 mps	
	$I$ proportional to $1 + R$ OR $I_{2\Omega} \times R_{2\Omega} = I_{4\Omega} \times R_{4\Omega}$	C1
	$I_{4\Omega} = I_{2\Omega} \div 2$	C1
	$(I_{4\Omega} = I_{2\Omega} \div 2 = 2.5 \div 2 =) 1.3\text{ A}$	C1
	Alternative route by potential divider	
	$V = IR$ in any form or $(V =) IR$ words, symbols or numbers	C1
	$(V_{2\Omega} = 2 \times 2.5 =) 5\text{ V}$	C1
	$V_T = 7.33 \times 5 \div 1.33 (= 27.51\text{ V})$	C1
	$(I_{6\Omega} = 27.51 \div 7.33 =) 3.8\text{ A}$	A1

Question	Answer	Marks
(b)	any sort of triangle symbol pointing to left in EF	B1
	a wire in CD	B1

22. 0625\_m19\_ms\_42 Q: 9

(a)	$I = V/R$ in any form OR $(R =) V/I$ OR $7.0/4.6$	C1
	$1.5\ \Omega$	A1
(b)	Resistor: resistance is constant	B1
	Thermistor: resistance decreases	B1
(c)(i)	$4.6 + 4.6$	C1
	$9.2\text{ A}$	A1
	OR Combined resistance = $(1.52^2 / (1.52 + 1.52) =) 0.76\ \Omega$	(C1)
	$(I =) 7.0 / 0.76 = 9.2\text{ A}$	(A1)
(c)(ii)	$(E =) IVt$ OR in words OR $9.2 \times 7 \times 5 \times 60$	C1
	$19000\text{ J}$	A1

23. 0625\_s19\_ms\_41 Q: 7

(a)	thermistor c.a.o.	<b>B1</b>
(b)(i)	$V_x = V_{30}$	<b>B1</b>
(b)(ii)	$V_x = E - V_{20}$ in any form	<b>B1</b>
(c)(i)	$1/R_1 + 1/R_2 = 1/R_{tot}$ OR $(R_{tot} =) R_1 R_2 / (R_1 + R_2)$ OR $1/15 + 1/30 = 1/R_{tot}$ OR $(15 \times 30) / (15 + 30)$	<b>C1</b>
	$10 (\Omega)$ OR $10 + 20$	<b>C1</b>
	$30 \Omega$	<b>A1</b>
(c)(ii)	$I = V / R$ in any form OR $(I =) V / R$ OR $6.0 / 30$	<b>C1</b>
	$0.20 \text{ A}$	<b>A1</b>
(d)	resistance of <u>X</u> decreases	<b>B1</b>
	ammeter reading / it increases and (total) resistance (of circuit) decreases / more voltage across $20 \Omega$ resistor	<b>B1</b>

24. 0625\_s19\_ms\_42 Q: 10

(a)	$1/R_p = 1/R_1 + 1/R_2$ OR $(R_p =) 1/(1/R_1 + 1/R_2)$ OR $(R_p =) R_1 R_2 / (R_1 + R_2)$ OR $(0.2 \times 0.3) / (0.2 + 0.3)$ OR $0.6 \times 0.2$	<b>C1</b>
	$(R_p =) 0.12 (\Omega)$	<b>C1</b>
	$(R_t = 0.12 \Omega + 0.20 \Omega =) 0.32 \Omega$	<b>A1</b>
(b)	Statement : resistance of lamp increases	<b>M1</b>
	Explanation : temperature of lamp increases	<b>A1</b>

25. 0625\_w19\_ms\_43 Q: 9

(a)(i)	voltmeter shown connected across LED	<b>B1</b>	
(a)(ii)	ammeter shown connected in series with LED	<b>B1</b>	
(b)	p.d. across two resistors in parallel = $(3.7 - 2.1 =) 1.6 \text{ V}$	resistance of circuit = $(3.7 / 0.19) = 19.5 \Omega$ AND resistance of LED = $(2.1 / 0.19) = 11.1 \Omega$	<b>B1</b>
	combined resistances of two resistors in parallel = $R/2$ OR $1/R = 1/R_1 + 1/R_2$ OR $R = R_1 R_2 / R_1 + R_2$ OR current in either $R = I/2$	resistance across parallel combination of resistors = $(19.5 - 11.1) = 8.4 \Omega$	<b>B1</b>
	$R = V / I$ in any form	$R = V / I$ in any form	<b>C1</b>
	$R/2 = 1.6 / 0.19$	$R/2 = 8.4 \Omega$	<b>C1</b>
	$17 \Omega$	$17 \Omega$	<b>A1</b>

26. 0625\_m18\_ms\_42 Q: 9

(a)(i)	Resistor: tick in 2nd box	<b>B1</b>
(a)(ii)	Lamp: tick in 1st box	<b>B1</b>
(b)	$(R =) V/I$ OR $(R =) 6.0/4.4$	<b>C1</b>
	$1.4 \Omega$	<b>A1</b>
(c)	Current in lamp = 4.4 A Current in resistor = 4.0 A	<b>C1</b>
	Current from supply (= 4.0 + 4.4) = 8.4 A	<b>A1</b>
	OR (With 6 V p.d.) $R_L = 6/4.4 = 1.36 \Omega$ $R_R = 6/4 = 1.5 \Omega$ Combined resistance = $(1.36 \times 1.5)/2.86 = 0.71 \Omega$	<b>(C1)</b>
	Current = $6/0.71 = 8.4$ A	<b>(A1)</b>
(d)	p.d. across lamp = 4.9 V p.d. across resistor = 6.0 V	<b>C1</b>
	Total p.d. (= 4.9 + 6.0) = 10.9 V	<b>A1</b>
	OR (With 4 A current) $R_L = 5/4 = 1.25 \Omega$ $R_R = 6/4 = 1.5 \Omega$ Total R = 2.75 $\Omega$	<b>(C1)</b>
	Total p.d. = $2.75 \times 4 = 11.0$ V	<b>(A1)</b>

27. 0625\_s18\_ms\_41 Q: 7

(a)	(Metals) contain free/mobile electrons/delocalised electrons	<b>1</b>
(b)(i)	$R \propto L$ and $R \propto 1/A$ OR $R \propto L/A$ OR $R = 16 \times \frac{1}{2} \div 2$ OR $R = 16 \div 4$	<b>1</b>
	$4.0 \Omega$	<b>1</b>
(b)(ii)	$1 + R = (1 + R_1) + (1 + R_2)$ OR $R = (R_1 \times R_2) \div (R_1 + R_2)$ OR $(1 + R) = (1 + 4) + (1 + 16)$ OR $(4 \times 16) \div (4 + 16)$	<b>1</b>
	$3.2 \Omega$	<b>1</b>
(c)(i)	$3E$ or $3 \times E$	<b>1</b>
(c)(ii)	$I_B > I_2 > I_1$ (6th box ticked)	<b>1</b>

28. 0625\_s18\_ms\_42 Q: 8

(a)(i)	variable resistor OR rheostat	<b>1</b>
(a)(ii)	voltmeter symbol correctly connected across $20 \Omega$ resistor	<b>1</b>
(b)	$(I = )V \div R$ OR $6.0 \div 20$ OR (any value $< 6.0$ ) $\div 20$	<b>1</b>
	correct calculation of I for $V > 0$ accept point on graph with correct co-ordinates, apart from the origin	<b>1</b>
	straight line from (0,0) to (6.0,0.30) tolerance within $\frac{1}{2}$ small square	<b>1</b>
(c)(i)	(combined resistance) less (than the resistance of either/smaller resistor)	<b>1</b>
(c)(ii)	steeper OR gradient greater OR description of how the line differs (e.g. reaches 0.40 A before V reaches 6.0 V) ignore 2nd line above 1st line	<b>1</b>

29. 0625\_s18\_ms\_43 Q: 9

(a)	$(R =) V \div I$ OR $12 \div 0.15$	<b>C1</b>
	$80 \Omega$	<b>A1</b>
(b)(i)	increases	<b>B1</b>
(b)(ii)	(voltmeter reading) decreases OR less p.d. across variable resistor	<b>B1</b>
	more p.d. across $20 \Omega$ /fixed resistor	<b>B1</b>
(c)(i)	<u>1.5 J</u> of (electrical) energy supplied in driving charge around the circuit	<b>B1</b>
	energy per unit charge OR per coulomb	<b>B1</b>
(c)(ii)	8	<b>B1</b>

30. 0625\_w18\_ms\_41 Q: 9

(a)	2 lamps with correct circuit symbol, in parallel, with correct connection to battery	<b>B1</b>
(b)(i)	$(12 / 6.0 =) 2.0 \text{ A}$	<b>B1</b>
(b)(ii)	$(P =) IV$ OR $2.0 \times 12$	<b>C1</b>
	OR $(P =) I^2 R$ OR $2.0^2 \times 6.0$	<b>(C1)</b>
	OR $(P =) V^2 / R$ OR $12^2 / 6.0$	<b>(C1)</b>
	24 W	<b>A1</b>
(c)	$(E =) IVt$ OR $Pt$ in any form OR $36 \times 20$	<b>C1</b>
	$= 36 \times 20 \times 60 \times 60$	<b>C1</b>
	$= 2.6 \times 10^6 \text{ J}$	<b>A1</b>

31. 0625\_w18\_ms\_42 Q: 7

(a)(i)	$P = I V$ in any form OR $(I =) P / V$	<b>C1</b>
	$(I = 60 / 110 =) 0.55 \text{ A}$	<b>A1</b>
(a)(ii)	$(I =) 1.6 \text{ A}$	<b>B1</b>
(a)(iii)	110 V	<b>B1</b>
(b)(i)	$I = V / R$ in any form OR $(R =) V / I$ OR $(R =) V^2 / P$ OR $(R =) P / I^2$	<b>C1</b>
	$(R = 110 / 0.55 =) 200 \Omega$	<b>A1</b>
(b)(ii)	2nd box (twice the length)	<b>B1</b>
	4th box (half the area of cross-section)	<b>B1</b>

32. 0625\_w18\_ms\_43 Q: 8


(a)	from chemical (energy) to thermal / heat (energy)	C1
	from chemical (energy) to thermal / heat (energy) and as a result of electrical working	A1
(b)(i)	$(I =) V/R$ or 2.4/120	C1
	0.020 A	A1
(b)(ii)	6.6 V	B1
(b)(iii)	330 $\Omega$	B1
(c)	multiplication by 5.0 or $R \propto l$	C1
	multiplication by 2.0/4.0 or division by 0.50/0.25 or $R \propto 1/A$ or $R \propto 1/r^2$	C1
	multiplication by 4.0 or division by 0.25 or $20 \times 330$	C1
	6600 $\Omega$	A1

33. 0625\_m17\_ms\_42 Q: 9

(a)(i)	Resistance constant	B1
(a)(ii)	Resistance increases	B1
(b)(i)	$I = V/R$ in any form OR $(R=) V/I$	C1
	8.0/0.72	C1
	11 $\Omega$	A1
(b)(ii)	$(P =) IV$ OR $0.72 \times 8.0$	C1
	5.8 W	A1
	OR $I^2R$ OR $0.72^2 \times$ candidate's (b)(i) OR $V^2/R$ OR $8^2 /$ candidate's (b)(i)	(C1)
	5.7 W or 5.8 W (dependent on exact data used)	(A1)
(c)(i)	8.0 V	B1
(c)(ii)	$(5 \times 0.72 =) 3.6$ A	B1
	<b>Total:</b>	<b>9</b>

AcelGCSE  
Paper Perfection, Crafted With Passion

34. 0625\_s17\_ms\_41 Q: 9

(a)(i)	LDR OR light-dependent resistor	<b>B1</b>
(a)(ii)		<b>B1</b>
(b)(i)	$I = V/R$	<b>C1</b>
	(total resistance =) 1.2 + 2.4 OR 3.6 seen	<b>C1</b>
	$I = 6.0/(1.2 + 2.4)$ OR 1.67 or 1.7 (mA)	<b>C1</b>
	(V =) 4.0 V	<b>A1</b>
	OR $(V_1) = [R_1 / (R_1 + R_2)] V$	<b>(C1)</b>
	(total resistance =) 1.2 + 2.4 OR 3.6 seen	<b>(C1)</b>
	$(V_1) = (2.4/3.6) 6.0$ = 4.0 V	<b>(A1)</b>
(b)(ii)	Replace the 1.2 k $\Omega$ resistor with one of higher value OR Increase the temperature (of the thermistor or the room)	<b>B1</b>
	<b>Total:</b>	<b>7</b>

35. 0625\_s17\_ms\_42 Q: 8

(a)(i)	$P=VI$ in any form OR $(I = ) P/V$	<b>C1</b>
	$(I = 9.0 / 6.0 = ) 1.5$ A	<b>A1</b>
(a)(ii)	$V=IR$ in any form OR $(R = ) V/I$ OR $P=V^2/R$ in any form OR $(R = ) V^2/P$	<b>C1</b>
	$(R = 6.0 / 1.5 = ) 4.0 \Omega$ or $(R = 36 / 9.0 = ) 4.0 \Omega$	<b>A1</b>
(b)(i)	resistance of wire is greater (than at X) OR current is less OR p.d. across lamp is less	<b>B1</b>
(b)(ii)	(for normal brightness of lamp, ) resistance of circuit (= $12 / 1.5$ ) = 8.0 $\Omega$	<b>C1</b>
	resistance of wire = $(8.0 - 4.0 = ) 4.0 \Omega$	<b>C1</b>
	(distance AX = $1.0 \times 4/5 = ) 0.80$ m OR (sliding contact is) 0.80 m (from A)	<b>A1</b>
	OR V across AX = 6.0 V	<b>(C1)</b>
	resistance of wire = $(6/\text{current from a(i)} = ) 4.0 \Omega$	<b>(C1)</b>
	(distance AX = $1.0 \times 4/5 = ) 0.80$ m OR (sliding contact is) 0.80 m (from A)	<b>(A1)</b>
	<b>Total:</b>	<b>8</b>

36. 0625\_s17\_ms\_43 Q: 9

(a)	$(I =) \frac{P}{V}$ OR $24 \div 6.0$ OR $4.0$ (A) OR $(R =) \frac{V}{I}$	C1
	$6.0 \div 4.0$	C1
	$1.5 \Omega$	A1
(b)(i)	6.0 V	B1
(b)(ii)	$1.5 \Omega$	B1
(b)(iii)	$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$ OR $1 \div 1.5 = \frac{1}{R_1} + \frac{1}{R_2}$ OR $1 \div 1.5 = \frac{2}{R}$	C1
	$3.0 (\Omega)$	A1
(c)	resistance of circuit/parallel pair increases	B1
	current (in lamp) decreases OR less p.d. across lamp	B1
<b>Total:</b>		<b>9</b>

37. 0625\_w17\_ms\_41 Q: 9

(a)(i)	$(3 \times 1.5 =) 4.5 V$	B1
(a)(ii)	$1/R = 1/R_1 + 1/R_2$ OR $R = 1/(1/R_1 + 1/R_2)$ OR $(R =) R_1 R_2 / (R_1 + R_2)$	C1
	Correct substitution of 3 and 6	C1
	$(R =) 2.0 \Omega$	A1
(a)(iii)	$V = IR$ in any form OR $(I =) V/R$ OR $4.5/3$	C1
	1.5 A	A1
	OR	
	$I_{total} = 4.5/2 = 2.25 A$	(C1)
	For $3 \Omega, I = 2.25 \times 6/9 = 1.5 A$	(A1)
(b)(i)	Connect ammeter (in wire) from A to B OR from H to G	B1
(b)(ii)	Connect voltmeter (terminals) to A and H OR B and G OR C and D OR E and F	B1

Paper Perfection, Crafted With Passion

38. 0625\_w17\_ms\_42 Q: 8

(a)	$R_S = R_A + R_B$ in any form OR $(R_S =) R_A + R_B$ OR $(R_S =) 4 + 8$	C1
	$(R_S =) 12 (\Omega)$	C1
	$(R_P =) 1/(1/R_S + 1/R_C)$ in any form OR $(R_P =) R_S R_C / (R_S + R_C)$ OR $(R_P =) 1/(1/12 + 1/6)$ OR $(R_P =) (6 \times 12)/18$	C1
	$(R_P =) 4.0 \Omega$	A1
(b)	$V_8 = \text{supply } V \times (8/12)$ OR $= 24 \times (8/12)$	C1
	$(V_8 =) 16 V$	A1
	OR alternative route	
	$I_8 = \text{supply } V / 12$ OR $= 24/12$ OR $= 2$ (A)	(C1)
	$(V_8 = 2 \times 8 =) 16 V$	(A1)